 


BLOCK DIAGRAM



FUNCTION TABLE

rst	clk_12MHz / 65536	lcd_data	lcd_rs	lcd_en
1	x	38h	0	x
0	↑	06h	0	↑
0	↑	0Ch	0	↑
0	↑	01h	0	↑
0	↑	50h (P)	1	↑
0	↑	49h (I)	1	↑
0	↑	43h (C)	1	↑
0	↑	54h (T)	1	↑
0	↑	20h ()	1	↑

MAIN VHDL MODEL (MVM)

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity LCD_FSM is
Port (    rst : in std_logic;           -- reset
        clk_12Mhz : in std_logic;      -- high freq. clock
        lcd_rs : out std_logic;         -- LCD RS control
        lcd_en : out std_logic;         -- LCD Enable
        lcd_data : out std_logic_vector(7 downto 0)); -- LCD Data port
end LCD_FSM;

architecture Behavioral of LCD_FSM is

    signal div : std_logic_vector(15 downto 0); --- delay timer 1
    signal clk_fsm,lcd_rs_s: std_logic;
    -- LCD controller FSM states
    type state is (reset,func,mode,cur,clear,d0,d1,d2,d3,d4,hold);
    signal ps1,nx : state;
    signal dataout_s : std_logic_vector(7 downto 0); --- internal data command multiplexer

begin

    ----- clk divider -----
    process(rst,clk_12Mhz)
    begin
        if(rst = '1')then
            div <= (others=>'0');
        elsif( clk_12Mhz'event and clk_12Mhz ='1')then

            div <= div + 1;
        end if;

    end process;

    -----
    clk_fsm <= div(15);

    ----- Presetn state Register -----
    process(rst,clk_fsm)
    begin
        if(rst = '1')then
            ps1 <= reset;
        elsif (rising_edge(clk_fsm)) then
            ps1 <= nx;

        end if;
    end process;
```

----- state and output decoding process

process(ps1)

begin

case(ps1) is

when reset =>

```
    nx      <= func;
    lcd_rs_s <= '0';
    dataout_s <= "00111000";    -- 38h
```

when func =>

```
    nx      <= mode;
    lcd_rs_s <= '0';
    dataout_s <= "00111000";    -- 38h
```

when mode =>

```
    nx      <= cur;
    lcd_rs_s <= '0';
    dataout_s <= "00000110";    -- 06h
```

when cur =>

```
    nx      <= clear;
    lcd_rs_s <= '0';
    dataout_s <= "00001100";    -- 0Ch curser at starting point of
```

line1

when clear=>

```
    nx      <= d0;
    lcd_rs_s <= '0';
    dataout_s <= "00000001";    -- 01h
```

when d0 =>

```
    lcd_rs_s <= '1';
    dataout_s <= "01010000";    -- P ( Decimal = 80 , HEX = 50 )
    nx      <= d1;
```

when d1 =>

```
    lcd_rs_s <= '1';
    dataout_s <= "01001001";    -- I ( Decimal = 73 , HEX = 49 )
    nx      <= d2;
```

when d2 =>

```
    lcd_rs_s <= '1';
    dataout_s <= "01000011";    -- C ( Decimal = 67 , HEX = 43 )
    nx      <= d3;
```

when d3 =>

```
    lcd_rs_s <= '1';
    dataout_s <= "01010100";    -- T ( Decimal = 84 , HEX = 54 )
    nx      <= d4;
```

```

when d4      =>
    lcd_rs_s    <= '1';
    dataout_s    <= "00100000";    -- space ( Decimal = 32 , HEX = 20 )
    nx          <= hold;

when hold    =>
    lcd_rs_s    <= '0';
    dataout_s    <= "00000000";    -- hold ( Decimal = 32 , HEX = 00 ) ,
NULL
    nx          <= hold;

when others=>
    nx          <= reset;
    lcd_rs_s    <= '0';
    dataout_s    <= "00000001";    -- CLEAR ( Decimal = 1 , HEX = 01 )

end case;
end process;

lcd_en <= clk_fsm;
lcd_rs <= lcd_rs_s;
lcd_data <= dataout_s;

end Behavioral;

```

TESTBENCH VHDL MODEL (TVM)

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY LCD_Test IS
END LCD_Test;

ARCHITECTURE behavior OF LCD_Test IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT LCD_FSM
    PORT(
        rst : IN std_logic;
        clk_12Mhz : IN std_logic;
        lcd_rs : OUT std_logic;
        lcd_en : OUT std_logic;
        lcd_data : OUT std_logic_vector(7 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal rst : std_logic := '0';
    signal clk_12Mhz : std_logic := '0';

    --Outputs
    signal lcd_rs : std_logic;
    signal lcd_en : std_logic;
    signal lcd_data : std_logic_vector(7 downto 0);

    -- Clock period definitions
    constant clk_12Mhz_period : time := 10 ns;

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: LCD_FSM PORT MAP (
        rst => rst,
        clk_12Mhz => clk_12Mhz,
        lcd_rs => lcd_rs,
        lcd_en => lcd_en,
        lcd_data => lcd_data
    );

    -- Clock process definitions
    clk_12Mhz_process : process
    begin
```

```
        clk_12Mhz <= '0';
        wait for clk_12Mhz_period/2;
        clk_12Mhz <= '1';
        wait for clk_12Mhz_period/2;
    end process;

    -- Stimulus process
    stim_proc: process
    begin
        rst <= '1';
        wait for 20 ns;

        rst <= '0';
        -- insert stimulus here

        wait;
    end process;

END;
```