 


**BLOCK DIAGRAM**



**Function Table:**

CLK	RST	rd_en	wr_en	data_in	fifo_empty	fifo_full	data_out
↑	1	X	X	X	1	0	(00) <sub>16</sub>
↑	0	0	1	(XY) <sub>16</sub>	0	0	(00) <sub>16</sub>
↑	0	1	0	(XY) <sub>16</sub>	0	1	(XY) <sub>16</sub>

## VHDL MODEL / PROGRAM

```
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
USE IEEE.NUMERIC_STD.ALL;
```

```
ENTITY FIFO is
generic (depth : integer := 16);
PORT (CLK : in std_logic;
      RST : in std_logic;
      rd_en : in std_logic;
      wr_en : in std_logic;
      data_in : in std_logic_vector(7 downto 0);
      data_out : out std_logic_vector(7 downto 0);
      fifo_empty : out std_logic;
      fifo_full : out std_logic
    );
END FIFO;
```

ARCHITECTURE FIFO\_arch of FIFO is

```
type memory_type is array (0 to depth-1) of std_logic_vector(7 downto 0);
signal memory : memory_type :=(others => (others => '0'));
signal readptr,writeptr : integer := 0;
signal empty,full : std_logic := '0';
```

begin

```
    fifo_empty <= empty;
    fifo_full <= full;
    process(CLK,RST)
    variable num_elem : integer := 0;
    begin
        if(RST = '1') then
            memory <= (others => (others=> '0'));
            data_out <= (others => '0');
            empty <= '1';
            full <= '0';
            readptr <= 0;
            writeptr <= 0;
            num_elem := 0;

            elsif(rising_edge(CLK)) then
                if(rd_en = '1' and empty = '0') then --read
                    data_out <= memory(readptr);
                    readptr <= readptr + 1;
                    num_elem := num_elem-1;
                end if;

                if(wr_en='1' and full = '0') then
                    memory(writeptr) <= data_in;
```

```

writeptr <= writeptr + 1;
num_elem := num_elem+1;
end if;

if(readptr = depth-1) then
    readptr <= 0;
end if;

if(writeptr = depth-1) then
    writeptr <= 0;
end if;

if(num_elem = 0) then
    empty <= '1';
else
    empty <= '0';
end if;

if(num_elem = depth) then
    full <= '1';
else
    full <= '0';
end if;
end if;
end process;
END FIFO_arch;
```

## FIFO TVM

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.std_logic_arith.ALL;

ENTITY fifo_tb IS
END fifo_tb;

ARCHITECTURE behavior OF fifo_tb IS
    --Inputs and outputs
    signal Clk,reset,enr,enw,empty,full : std_logic := '0';
    signal data_in,data_out : std_logic_vector(7 downto 0) := (others => '0');
    --temporary signals
    signal i : integer := 0;
    -- Clock period definitions
    constant Clk_period : time := 10 ns;
    constant depth : integer := 16; --specify depth of fifo here.

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: entity work.fifo generic map(depth => depth) PORT MAP
    (clk,reset,enr,enw,data_in,data_out,empty,full);

    -- Clock process definitions
    Clk_process :process
    begin
        Clk <= '0';
        wait for Clk_period/2;
        Clk <= '1';
        wait for Clk_period/2;
    end process;

    -- Stimulus process
    stim_proc: process
    begin
        reset <= '1'; --apply reset for one clock cycle.
        wait for clk_period;
        reset <= '0';
        wait for clk_period*3; --wait for 3 clock periods(simply)
        enw <= '1';  enr <= '0';    --write 10 values to fifo.
        for i in 1 to 10 loop
            Data_In <= conv_std_logic_vector(i,8);
            wait for clk_period;
        end loop;
        enw <= '0';  enr <= '1';    --read 4 values from fifo.
        wait for clk_period*4;
        enw <= '0';  enr <= '0';
        wait for clk_period*10; --wait for some clock cycles.
        enw <= '1';  enr <= '0';    --write 10 values to fifo.
```

```

for i in 11 to 20 loop
    Data_In <= conv_std_logic_vector(i,8);
    wait for clk_period;
end loop;
enw <= '0';  enr <= '0';
wait for clk_period*10; --wait for some clock cycles.
enw <= '0';  enr <= '1';    --read 4 values from fifo.
wait for clk_period*4;
enw <= '0';  enr <= '0';
wait for clk_period;
enw <= '0';  enr <= '1';    --read 4 values from fifo.
wait for clk_period*8;
enw <= '0';  enr <= '0';
wait for clk_period;
enw <= '0';  enr <= '1';    --read 8 values from fifo.
wait for clk_period*4;
enw <= '0';  enr <= '0';
wait for clk_period;
enw <= '0';  enr <= '1';    --read 4 values from fifo.
wait for clk_period*4;
enw <= '0';  enr <= '0';
wait;
end process;

END;

```